


## HOMework #2

*(Due: Thursday, October 12, 2017, 11:59 pm PT via Gradescope Online Submission)*

1. **Quick Questions.** For each of the following statements, state “T” for true or “F” for false. No explanation necessary. Correct answers are worth +1 point, while incorrect answers yield -1 point. No points for unanswered questions. Your minimum total score on this problem is zero points.

a) In a D/A interface, the images from first-order hold reconstruction can be removed using an appropriate digital filter at the DAC input.	
b) A D/A interface that is built using an oversampling delta-sigma loop does not require a DAC in its feedback path.	
c) It is not possible to have $DNL = -1.5$ LSB in a thermometer D/A converter.	

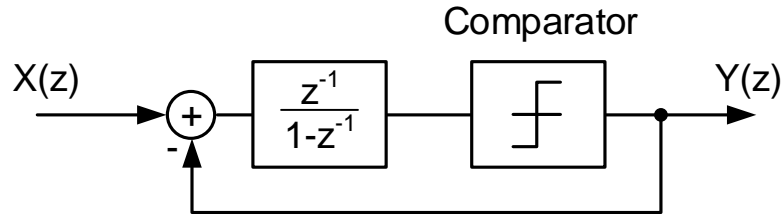2. **Matlab simulation of a basic delta-sigma converter.** Consider the first-order, single-bit delta-sigma modulator shown below.



- a) Download the starter file “hw2\_ds.m” from the course website (under “homework”). This program is meant to simulate the system with a DC input and compute the average of the digital output. Complete the code and try a number of different DC inputs: 0.5, 0.8,  $-0.2$ . Verify that the cumulative average of the output converges to the DC input over time. Submit the Matlab plot for  $X = 0.8$ .
  - b) What happens when you have a DC input larger than 1? Explain the observed behavior (The output  $Y(z)$  and well as the internal output of the integrator).
  - c) Modify the Matlab program to simulate the converter with a sine-wave input. Use a half-scale sine wave with 5 cycles in 4096 points and then take the FFT of the output. What is the oversampling ratio assuming that the sinusoid frequency corresponds to the signal band edge ( $f_B$ )? Plot the magnitude FFT in dBFS, where the full scale range is defined by the  $+1/-1$  feedback levels. Scale the x-axis of the plot to reflect the normalized frequency  $f/f_s$ . Verify the existence of noise-shaping and submit your FFT plot.
  - d) From the FFT output, extract the quantization noise power in the band from 0 to  $0.05f_s$  (do not include the signal bin!). What is the value you would expect from first order theory? Comment on the potential discrepancies.
3. A segmented DAC consists of a thermometer encoded MSB DAC with 6 bits. The standard deviation of the elements from their nominal value is 3%. The number of bits in the binary weighted LSB DAC is 6 bits and the standard deviation of the elements is 4%. What is the standard deviation of the DNL for the worst code?

4. Read the following paper: C.-H. Lin and K. Bult, "A 10-b, 500-MSample/s CMOS DAC in 0.6  $\mu\text{m}^2$ ," IEEE J. Solid-State Circuits, vol. 33, pp. 1948-1958, Dec. 1998. What application is this DAC intended for?
5. In the above reference, it was found that for the given objectives, a thermometer/binary partition of 8/2 is most suitable. Your task in this problem is to re-optimize this DAC for a 65-nm technology with a different set of process parameters, without altering its basic structure. The design variables to be optimized are:

Parameter	Description
$B_t$	Number of bits in thermometer section
$A_{\text{unit}}$	Area of unit current source

Your target specs and process parameters are:

Parameter	Description	Value
B	Resolution	12 bits
$\text{INL}_{\text{spec}}$	Worst case integral nonlinearity	$< 0.5 \text{ LSB}$
$\text{DNL}_{\text{spec}}$	Worst case differential nonlinearity	$< 0.5 \text{ LSB}$
Y	Target yield	95%
$A_{\text{decode}}$	Approximate decoder and routing area	$2^{B_t} \cdot 2000 \mu\text{m}^2$
$A_{\text{total}}$	Total DAC area (to be minimized)	$2^B \cdot A_{\text{unit}} + A_{\text{decode}}$
$k_u$	Unit element matching parameter	$6\% \mu\text{m}$
$\sigma_u$	Standard deviation of unit element mismatch	$k_u / \sqrt{A_{\text{unit}}}$

- a) Following the procedure outlined in the reference, answer the following **using only hand calculations** (After the equations are written by hand, it is ok to use Matlab/ Excel to perform a sweep across **integer** values of  $B_t$ ):
  - i. What values of  $A_{\text{unit}}$  and  $B_t$  actually minimize the total area defined above in the table? What is the minimum total area (in  $\text{mm}^2$ )?
  - ii. What values of  $A_{\text{unit}}$  and  $B_t$  give the "optimal point" described by the paper? What is the total area (in  $\text{mm}^2$ ) in this case
- b) Create a plot similar to Fig. 9 of the reference paper to illustrate the "minimum area" design. In this diagram, plot the total DAC area in  $\text{mm}^2$  (log scale) versus the design parameter  $B_t$  (linear scale in bits).
6. Use Matlab to simulate your "minimum area" design from problem 5 part (a) i, and make appropriate modifications to achieve the targeted yield.
  - a) Download the starter file "hw2\_dac.m" from the "Homework" section of the course website. This file contains code for a 100-run Monte Carlo simulation that generates an INL envelope and RMS plot (see Fig. 7 and Fig. 8 of the paper). Below the line "Your code goes here," add additional code to generate the respective plots also for DNL. Turn in a printout of the code you added to the file (no need to submit a printout of the given code).

- b) Generate and turn in envelope and RMS plots for both DNL and INL using the parameters you calculated in your hand analysis. Note that you should use the  $A_{\text{unit}}$  and  $B_t$  values calculated above in problem 4.
- c) Does your initial design meet the yield spec? Explain why it does or why it doesn't. Note that meeting the yield spec requires that “on average” no more than 5 out of the 100 runs lie outside the specified DNL or INL.
- d) If your hand design does not meet the yield spec, make appropriate adjustments (OK to iterate in Matlab) to  $A_{\text{unit}}$  without changing anything else. What is the value of  $A_{\text{unit}}$  that achieves the desired yield? What is the final total area of your design?