

# Review Session 3



10/13/2017

# Corn Remote Connections


- VNC Issues?
- Try X11 Forwarding
  - Windows:
    - PuTTY: <http://www.putty.org/>
    - Xming: <https://sourceforge.net/projects/xming/>
  - MAC:
    - XQuartz: <https://www.xquartz.org/>
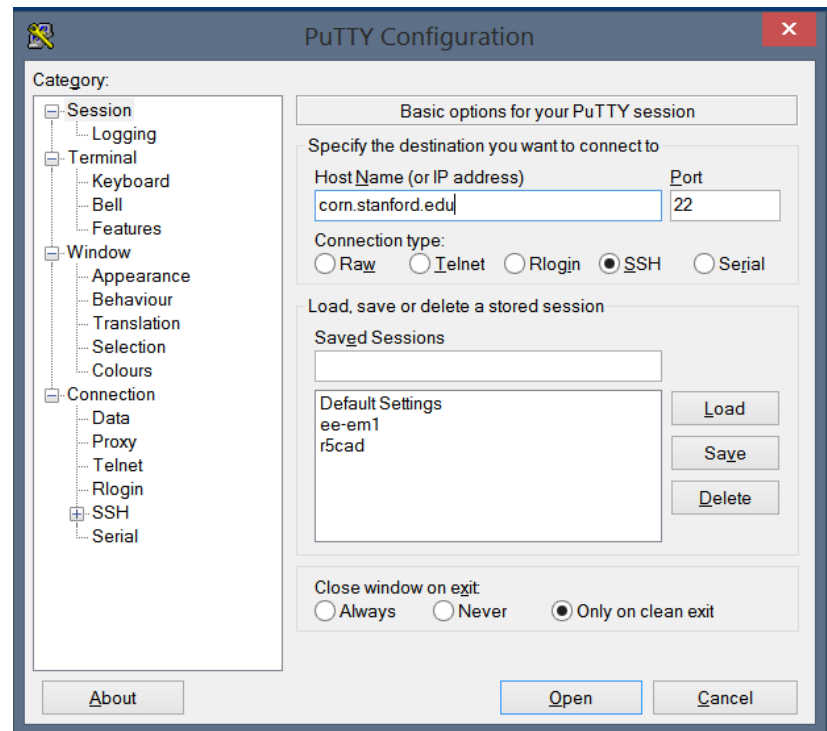 
# Windows: SSH with X11 Forwarding

- Run Xming, then connect to corn through PuTTY




# Windows: SSH with X11 Forwarding

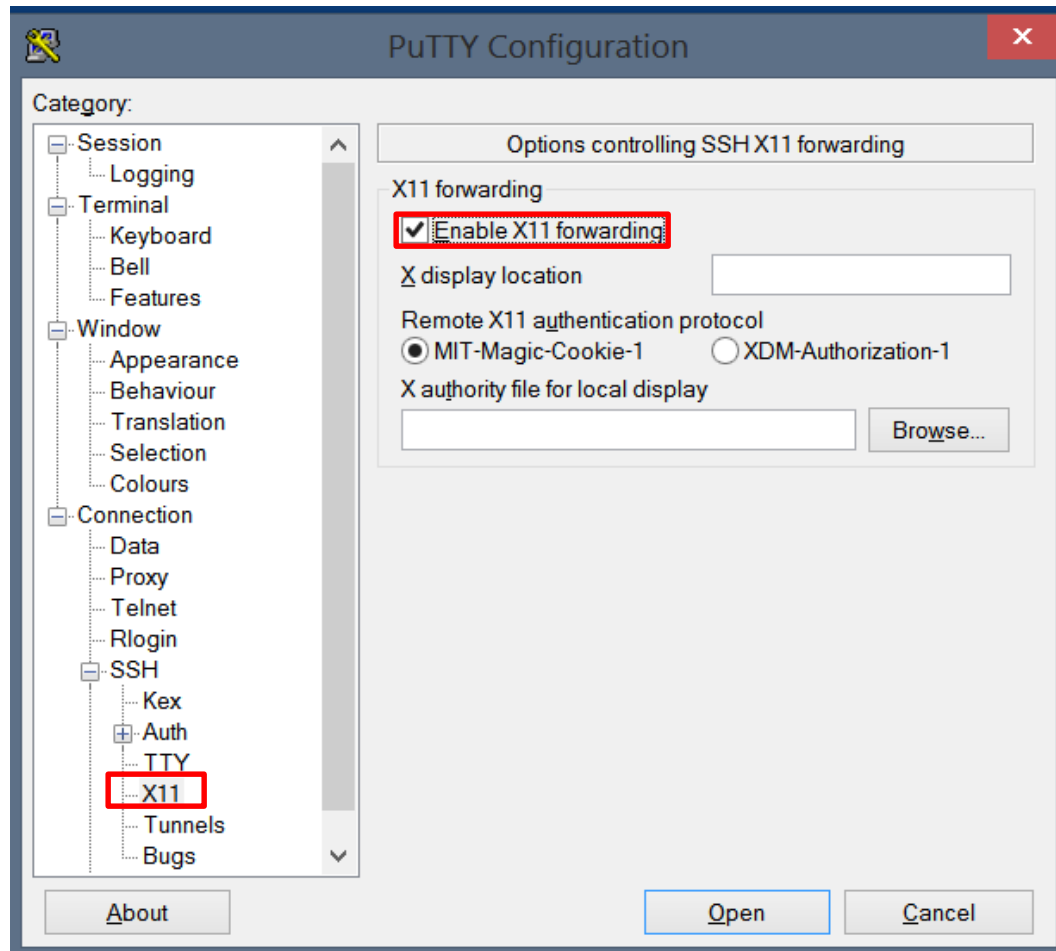

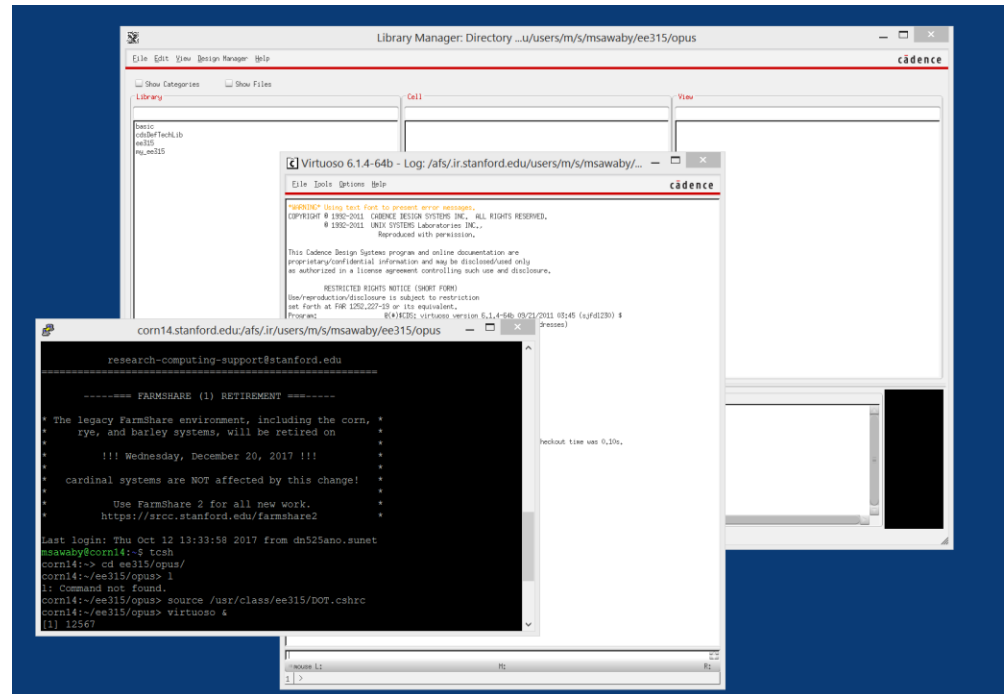
# Windows: SSH with X11 Forwarding

- In the shell that opens:
  - Log in.
  - Load virtuosso like usual (as if you are logging through corn.)




# MAC: X11 Forwarding

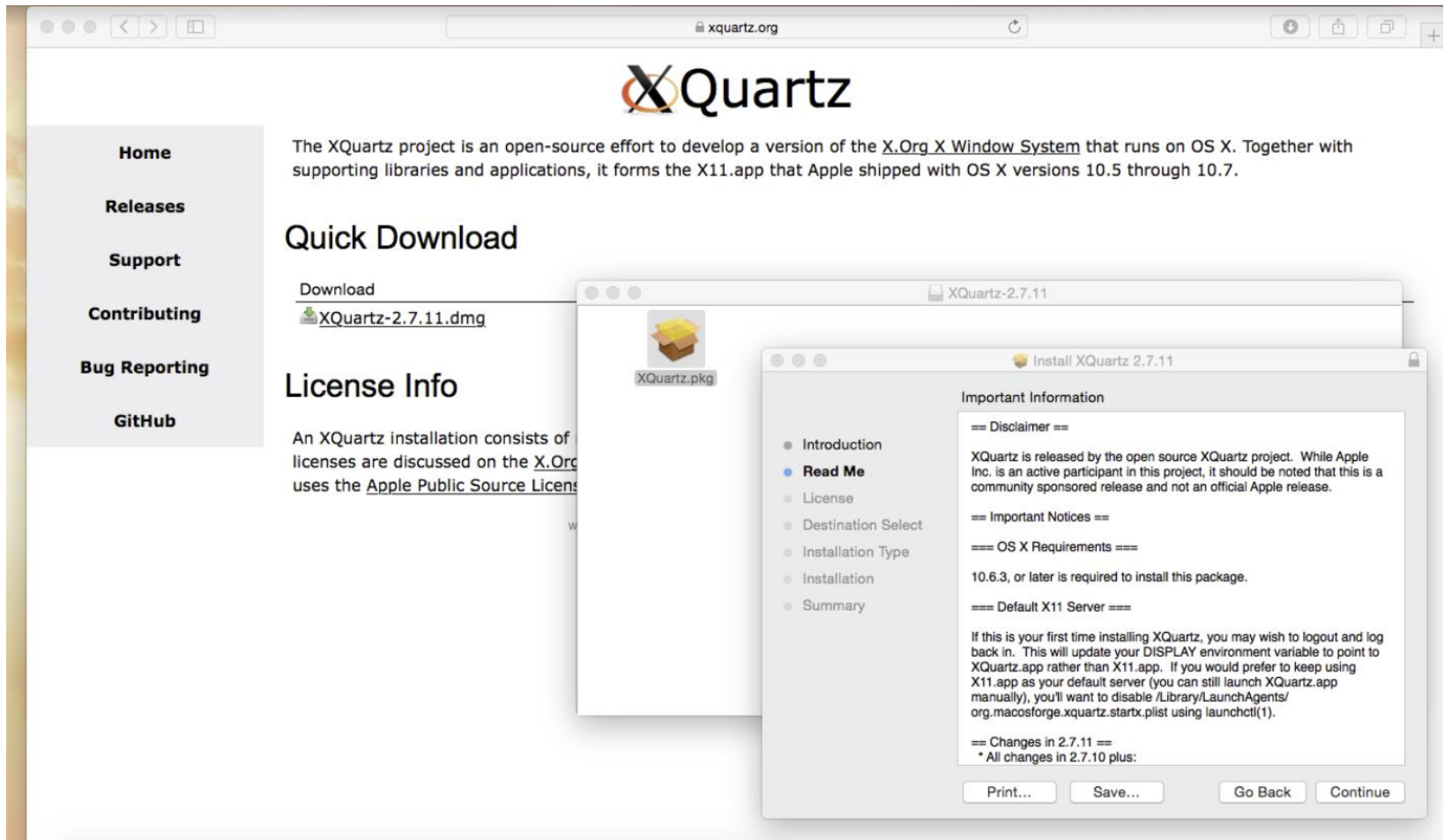
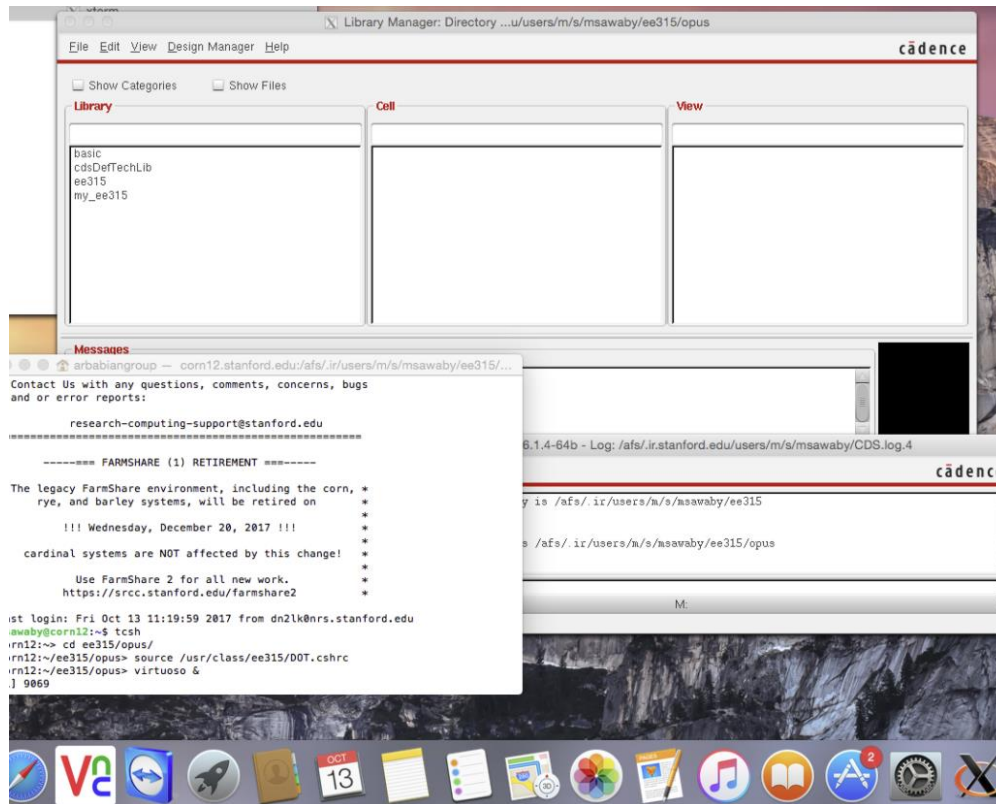
# MAC: X11 Forwarding

- Lunch XQuartz. In a terminal, type:
  - `ssh -X corn.stanford.edu -l msawaby`



# HW3

*Submission through Gradescope*

Q1: T/F

Q2: ADC Performance

Q3: Switch ON Resistance

Q4: Switch Non-Idealities

Q5: CAD



Q6: Bottom-Plate Sampling





## Q2 Hint

- Plot spectrum, get input freq.
- Calculate SNR, SNDR, ENOB, THD: write your own code!
- Part e) the ADC has ideal  $\Delta^2/12$  quantization noise. Noise sources are thermal and quantization.

# Q3 Review: Tracking Nonlinearity

  

 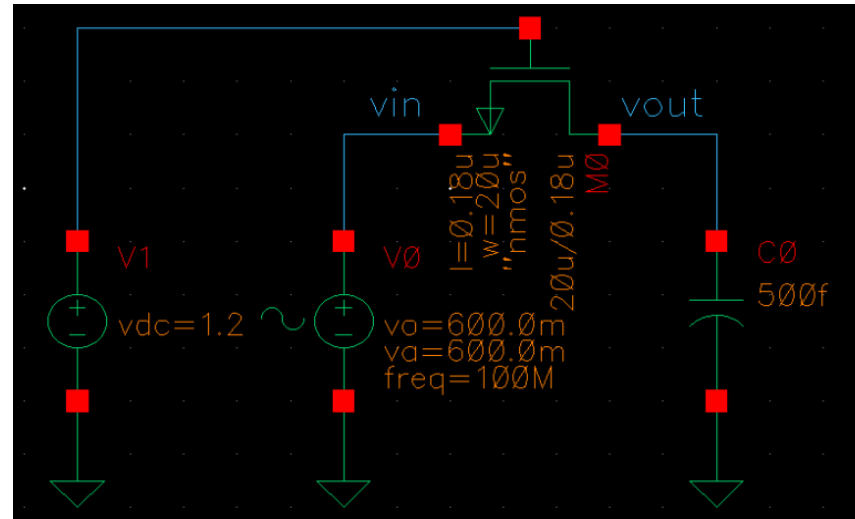
Razavi, Data Conversion System Design, p.16



# Q3 Review: Tracking Nonlinearity


- Transmission gate

added pmos, same dimensions as nmos

 


- Bootstrapped NMOS

added vdc to  
set  $V_{gs}=V_{dd}$

 

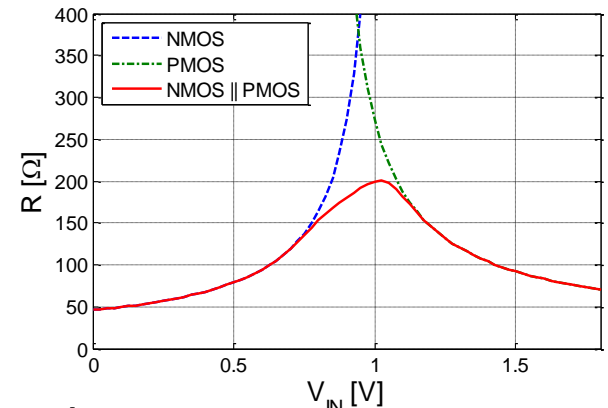
# Q3 Hint

- Simulation using Cadence
- Recall how t-gate works (lecture 5-6, slide 31)
- Recommend to start this problem early in case corn goes down
- Suggestion: plot using Matlab
- Condition to minimize variation?
  - Theory
  - From sims:  $R_{on} \text{ variation} = \max(R_{on})/\min(R_{on})$   
(use  $r_{on} = 1/g_{ds}$  and not  $r_{on}$  directly!)
  - No need to re-simulate: scale  $R_{on}$ !


 
# Q4 Review

- Calculate Noise (std deviation of signal), charge injection and clock feedthrough.
- Let's solve this example:



# Switched Cap Noise Example

- During  $\Phi_1$  after redistribution in  $\Phi_2$ :


$$-\frac{kT}{C_1} \left( \frac{C_1}{C_1+C_2} \right)^2 + \frac{kT}{C_2} \left( \frac{C_2}{C_1+C_2} \right)^2$$

- During  $\Phi_2$ ,  $C_1$  and  $C_2$  are in series:

$$-\frac{kT}{\frac{C_1 C_2}{C_1+C_2}} \left( \frac{C_1}{C_1+C_2} \right)^2$$

- Adding all we get:

$$-\frac{kT}{C_2}$$

 

# Problem 6



- Hand calculate, then simulate bottom plate sampling circuit
  - Charge injection, Noise, Distortion
  - For NMOS parameters, run DC simulation then plot DC op through (results -> print -> DC Operating Points) then click on the transistor. (or assume:  $C_{ox}=10\text{fF}/\mu\text{m}^2$ ,  $V_t=0.6\text{V}$ )
- Noise simulation: pss, pnoise
  - Models as LPTV circuit, gets a result using a single simulation
  - Downside: simulation is slow, because you need so many sidebands (due to high N)

# Problem 6


- Can also simulate using .noise
  - One simulation for each phase; add up the powers
  - Simulation files are switch\_cap\_ckt\_noise in ee315 library
- Different capacitances and OTA input-referred noise so these numbers differ from your homework




# Schematic

 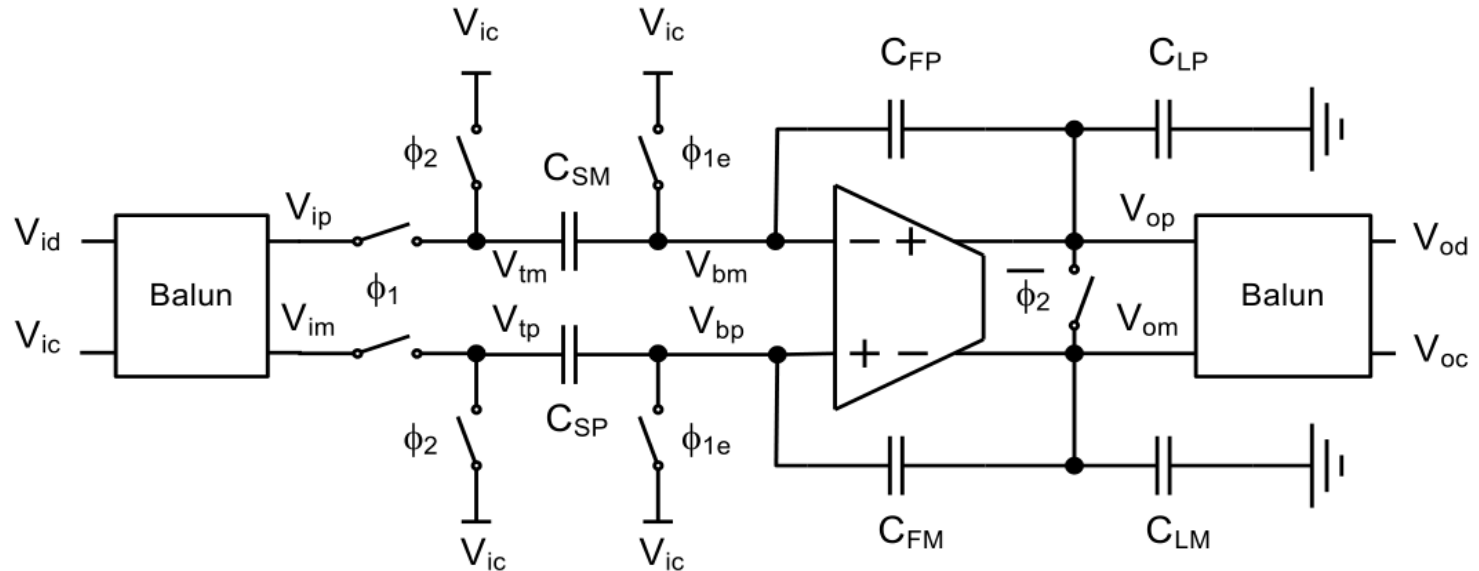

# Two Phases

 

Noise due to switches

 

Noise due to amplifier and switches



Reference: Murmann, Solid-State Circuits Magazine, 6/2012

# Phase 1: Tracking

- Interested in the total noise charge at input to the OTA
- What do we know?
  - Capacitance
  - Voltage
- We will have to calculate the charge ourselves with voltage-controlled voltage sources (VCVS)
- $Q_{\text{tot}} = C_s * V_s + C_x * V_x + C_f * V_f$ 
  - $V_s$  = voltage across capacitor  $C_s$
  - $C_x$  adds to the total noise charge (Also affects feedback factor!)
- Note: we'll find single-ended noise, then double it to get differential noise

 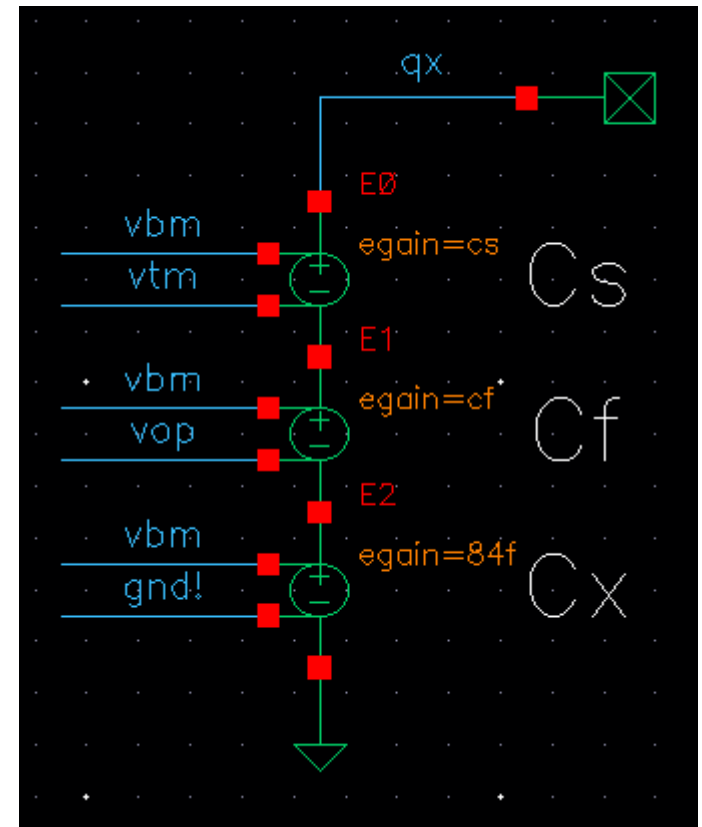
# Phase 1: How to measure Qx

- VCVS produces an output equal to:
  - $V_{out} = e_{gain} * (V_+ - V_-)$
- With  $e_{gain}=C$ , the output “voltage” is really representing the charge
- Example: voltage across  $C_s$  will be  $v_{bm} - v_{tm}$


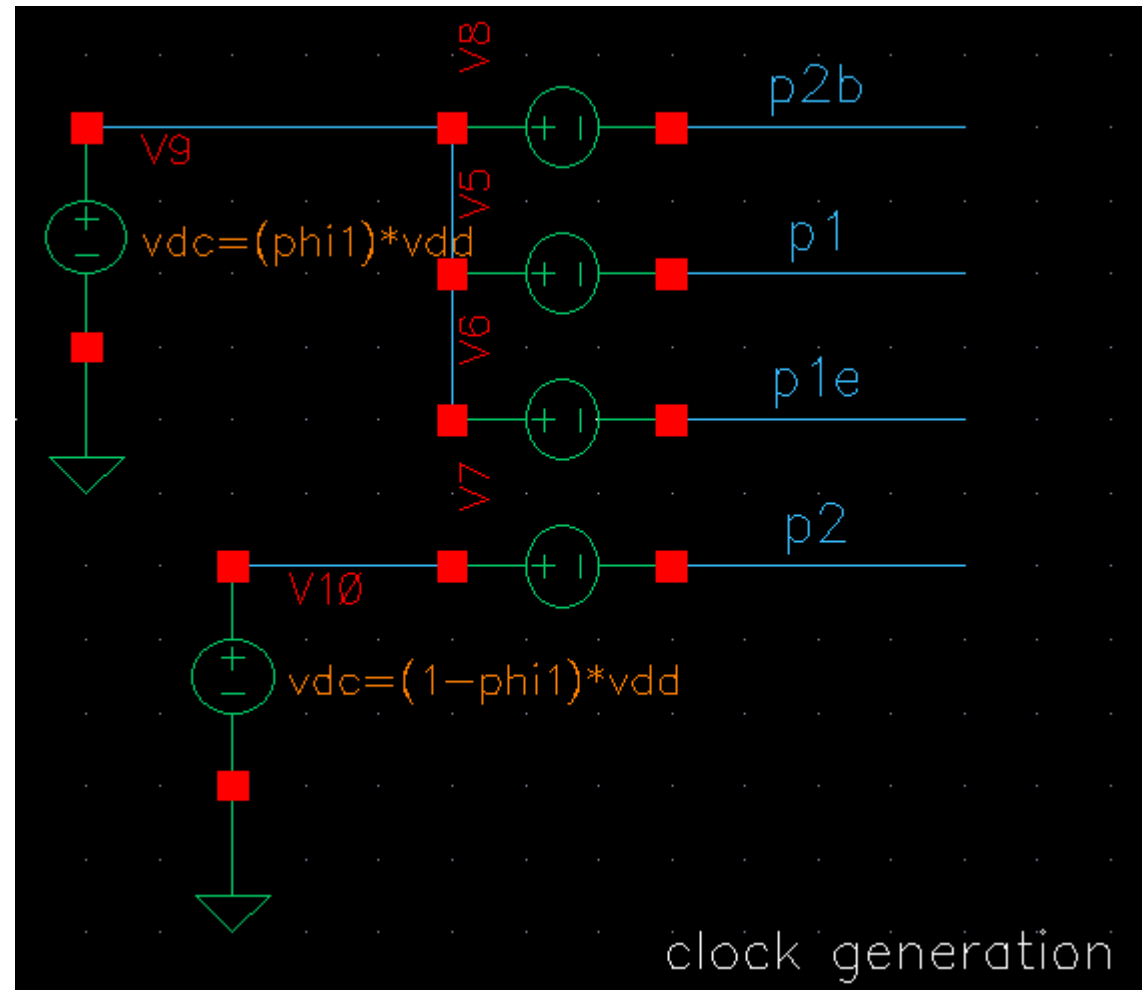
# Phase 1: Switch configuration

- Easily change clock phases from ADE L window



# Phase 1: Schematic summary

- Summary so far...
  - We want to sum up the charge at node X
  - To do this, we use VCVS to measure the voltage across each capacitor, and use  $Q=CV$  to calculate the charge across that capacitor
- Next
  - Set up the .noise analysis

# Phase 1: Tracking

- Design variables copied from the pss/pnoise analysis from before
  - Add “phi1 = 1”
- Noise analysis:
  - Sweep freq 1M-10T
  - Output from /qx to /gnd!
  - No input source

The image shows a configuration window for a noise analysis. It is divided into several sections:

- Sweep Variable:** Contains five radio buttons. "Frequency" is selected, while "Design Variable", "Temperature", "Component Parameter", and "Model Parameter" are unselected.
- Sweep Range:** Contains two radio buttons. "Start-Stop" is selected, and "Center-Span" is unselected. To the right of the "Start-Stop" radio are two text input fields: "Start" with the value "1M" and "Stop" with the value "1P".
- Sweep Type:** A dropdown menu showing "Automatic" with a red arrow icon to its right.
- Add Specific Points:** A checkbox that is currently unchecked.
- Output Noise:** Contains a dropdown menu showing "voltage" with a red arrow icon to its right. To the right of this dropdown are two rows of controls:
  - Positive Output Node:** A text input field containing "/qx" and a "Select" button to its right.
  - Negative Output Node:** A text input field containing "/gnd!" and a "Select" button to its right.
- Input Noise:** A dropdown menu showing "none" with a red arrow icon to its right.



# Phase 1: Calculating output noise

- The output from .noise is the charge noise power at node X (units are Coulomb<sup>2</sup>/Hz)
  - Cadence thinks the units are V<sup>2</sup>/Hz, but it's wrong. Recall we scaled the capacitor voltages by capacitance, so it's really charge noise that we're getting
- $V^2 = Q^2 / C^2$ , so we get output-referred voltage noise using

$$VN2() / \text{pow}(\text{VAR}("cf"), 2)$$



# Phase 1: Plotting output noise

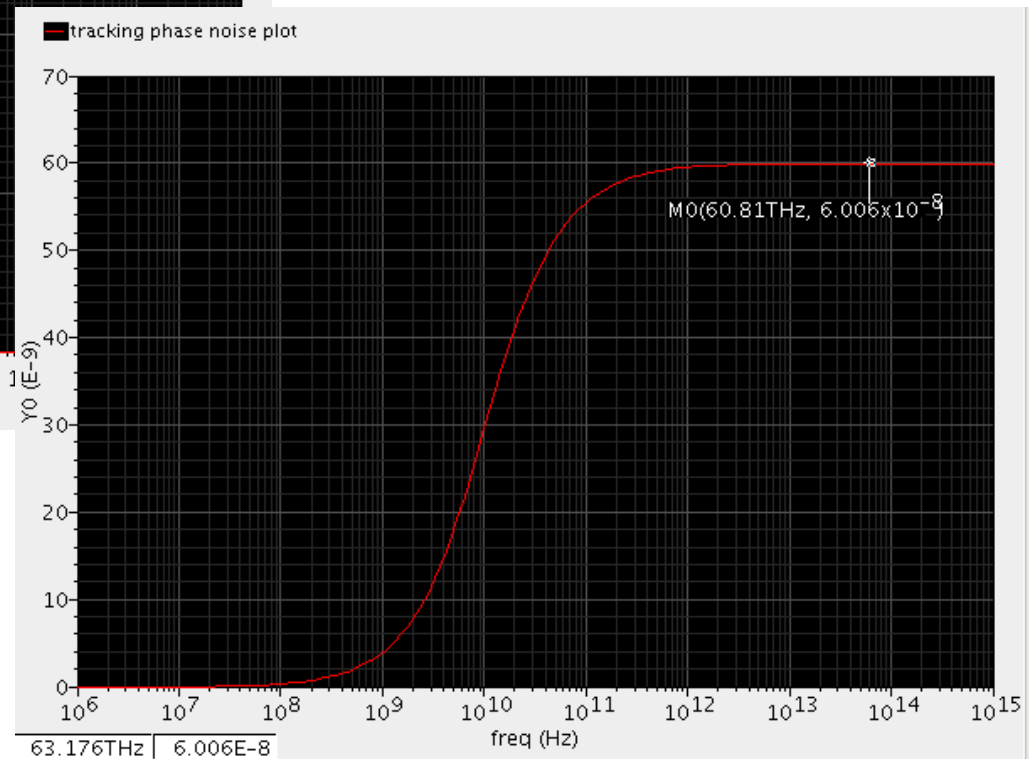 

# Phase 1: Hand calcs


- Recall factor of 2 to get differential noise
- Hand calculation:  $1.14 * 10^{-7} \text{ V}^2$
- Simulation:  $1.20 * 10^{-7} \text{ V}^2$

# Phase 2: Configuration

- Change variable  $\phi_1=0$  to put us in phase 2
- Change .noise output to /vod to /gnd!  
(differential noise)
- Output no longer needs scaling by  $C_f^2$

```
iinteg(VN2 ( ) )
```

# Phase 2: Plotting

 


## Phase 2: Hand calcs

- Hand calculation:  $6.6 * 10^{-8} \text{ V}^2$
- Simulation:  $5.9 * 10^{-8} \text{ V}^2$

# PSS Simulation

## PSS Simulation Setup

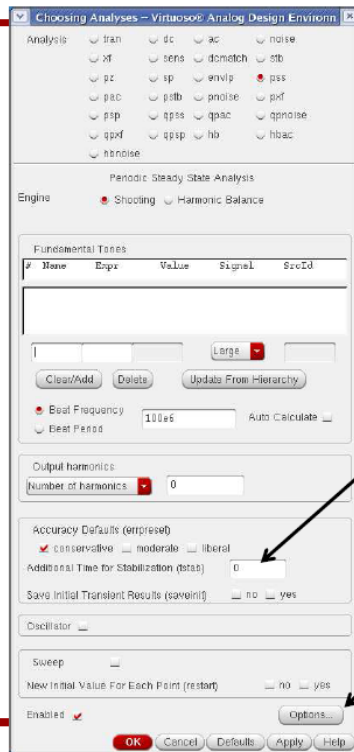

Set "tstab" if your circuit needs time to reach steady state (e.g. clock bootstrap circuits)

Under "options" set "maxacfreq" to the highest frequency from which you expect noise to fold down

# Comparison

	Phase 1 noise	Phase 2 noise	Total noise
Hand calculation	1.14e-7	6.6e-8	1.80e-7
Simulation .noise	1.20e-7	5.9e-8	1.79e-7
Simulation .pnoise (500 sidebands)	1.07e-7	5.6e-8	1.63e-7
Simulation .pnoise (2000 sidebands)	1.15E-7	5.6e-8	1.71e-7