

1) a) F

b) T

c) T


2) a) ① $Q_{in,CT}(t) = \int_{t-DT_s}^t I_{out,ld}(t') dt'$

D = Duty Cycle $T_s = 1/f_s \rightarrow$ (sc clock period)

$I_{out,ld}$ = Differential output current from A_1

$Q_{in,CT}$ = Running windowed integral of $I_{out,ld}$

$I_{out,ld}$ convolved with rectangle height 1, width $D \cdot T_s$

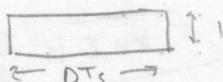rectangle \rightarrow 

$$\text{rect}(x) = h \cdot \Pi\left(\frac{x-c}{b}\right) \quad c = \text{center} = \frac{D \cdot T_s}{2} \quad b = \text{width} = D \cdot T_s$$

$$h = \text{height} = 1 \quad x = t - t'$$

$$Q_{in,CT}(t) = \int_{-\infty}^{\infty} \Pi\left(\frac{t - \frac{D \cdot T_s}{2} - t'}{D \cdot T_s}\right) \cdot I_{out,ld}(t') dt'$$

$$\int_{-\infty}^{\infty} x(t') dt' = x(t)$$

$$Q_{in,CT}(t) = I_{out,ld}(t) \cdot \Pi\left(\frac{t - \frac{D \cdot T_s}{2}}{D \cdot T_s}\right)$$

$$|Q_{in,CT}(\omega)| = |\mathcal{F}(I_{out,ld}(t) \cdot \Pi(\frac{t - \frac{D \cdot T_s}{2}}{D \cdot T_s}))|$$

$$= |I_{out,ld}(\omega)| \cdot \left| \int_{-\infty}^{\infty} e^{-j\omega t} \Pi\left(\frac{t - \frac{D \cdot T_s}{2}}{D \cdot T_s}\right) dt \right|$$

$$= |I_{out,ld}(\omega)| \cdot \left| \int_{-DT_s}^{DT_s} e^{-j\omega t} dt \right| \Rightarrow \frac{-1}{j\omega} (e^{-j\omega DT_s} - e^{j\omega DT_s})$$

$$\sin(\omega) = \frac{1}{2j} (e^{j\omega} - e^{-j\omega})$$



$$= \left| \frac{1}{j\omega} (e^{j\omega DT_s} - e^{-j\omega DT_s}) \right| = \left| \frac{2 \cdot \sin(\omega DT_s)}{\omega} \right| \cdot |I_{out,ld}(\omega)|$$

② $\frac{|Q_{in,CT}(\omega)|}{|I_{out,ld}(\omega)|} = \left| \frac{2 \cdot \sin(\omega DT_s)}{\omega} \right|$

2) b) WEB of sine prefilter 3.4x smaller than voltage sampling designed for 0.1% settling in DT_s

error @ $t = nT_s = 0.1\%$

$n = -\ln(0.1\%) = 6.90$

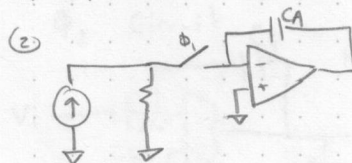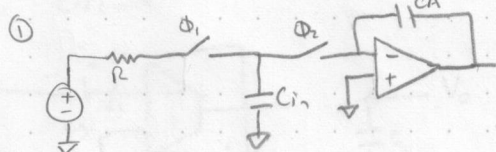

$$ENBW_1 = \frac{KT}{C} \cdot \frac{1}{4kTn} = \frac{1}{4RC}$$

$$DT_s = n \cdot T_s = n \cdot R \cdot C \quad RC = \frac{DT_s}{n}$$


$$ENBW_1 = \frac{n}{4DT_s} =$$

(2) Boxcar sampler - $ENBW_2 = \frac{f_s}{2} = \frac{1}{2DT_s}$

$$\frac{ENBW_1}{ENBW_2} = \frac{\frac{n}{4DT_s}}{\frac{1}{2DT_s}} = \frac{n}{2} = 3.45$$

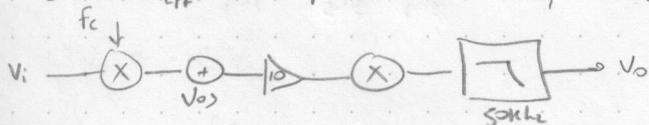
3) $A=10$ $BW \rightarrow$ $Z_{in} = \infty$ $Z_{out} = 0$ $V_{os} = 20mV$ $f_c = 1MHz$ $f_{LFF} = 50kHz$

$f_c = 20 \cdot f_{LFF}$ on period of $\frac{1}{2}T_c$, step response looks like triangle wave



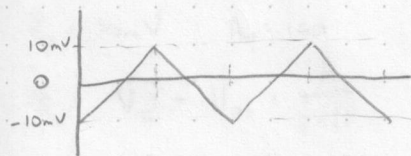a) $V_i = 0$, plot V_o

$V_{os} \cdot 10 = 200mV$ @ $1MHz$, 1 pole - gain = $\frac{1}{\sqrt{1 + \frac{1MHz^2}{50kHz^2}}} = 0.05$
 $V_p = V_{os} \cdot 10 \cdot 0.05 = 0.01V$




b) $V_{pp} = 2 \cdot V_p$ $V_p = 10mV$ $V_{pp} = 20mV$


4) $f_{clk} = 10 \text{ MHz}$ $T_{\phi_1} = T_{\phi_2} = \frac{T_{clk}}{2}$ $C_s = C_L = 2 \text{ pF}$ $C_f = 1 \text{ pF}$ $G_m = 1 \text{ mS}$ $r = 1$ $\alpha = 3$

a) Voltage gain from V_i to V_o

ϕ_1 circuit

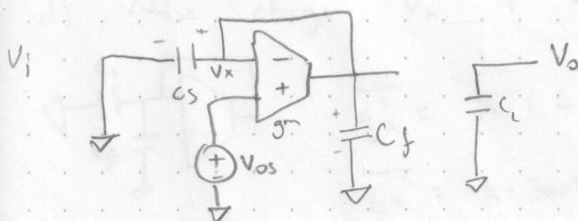

ϕ_2 circuit

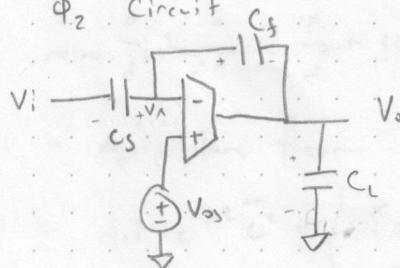

$$Q = C \cdot V_c$$

$$Q_L = C_L \cdot V_o$$

$$V_x \approx \text{Virtual Gnd} \approx V_{os}$$

$$\phi_1, V_{cs} = V_{cf} = V_{os} \quad Q_x = 0$$

$$\phi_2, V_{cs} = V_x - V_i \quad V_{cf} = V_x - V_o \quad Q_x = 0$$

$$Q_x = 0 = C_s(V_x - V_i) + C_f(V_x - V_o) = C_s V_x - C_s V_i + C_f V_x - C_f V_o$$

$$C_f V_o = C_s V_x - C_s V_i + C_f V_x = V_x(C_s + C_f) - C_s V_i$$

$$V_x = V_{os} \approx 0$$

$$C_f V_o = -C_s V_i$$

$$\frac{V_o}{V_i} = -\frac{C_s}{C_f} = -\frac{2 \text{ pF}}{1 \text{ pF}} = -2$$

b) $V_{os} = 10 \text{ mV}$ $A_v = 100$

$$\phi_1, V_c = V_{os} \cdot \frac{A}{1+A}$$

$$\phi_2, V_o = A(V_{in} - V_c + V_{os}) = A(V_{in} - V_{os} \frac{A}{1+A} + V_{os})$$

$$V_o = A V_{in} + A V_{os} \left(1 - \frac{A}{1+A}\right) \Rightarrow A \left(1 - \frac{A}{1+A}\right) = A - \frac{A^2}{1+A} = 0.99$$

$$V_o = A V_{in} + 0.99 V_{os} - \beta V_o \quad \beta = \frac{C_f}{C_f + C_s} = \frac{1}{3}$$

$$V_o + \beta V_o = A V_{in} + 0.99 V_{os}$$

$$V_o (1 + \beta) = A V_{in} + 0.99 V_{os}$$


$$V_o = \frac{A V_{in} + 0.99 V_{os}}{1 + \beta} \quad \begin{matrix} V_i = 0, & V_{os} = 0.99 \\ V_o = & \frac{V_{os}}{1 + \beta} \end{matrix}$$

$$\text{Input referred noise} \sim \frac{V_{os}}{A}$$

4) c) V_{os} - slow drift 1Hz sinusoid $A = 1mV$

For $A \rightarrow \infty$, input referred amplitude $\approx 1mV$

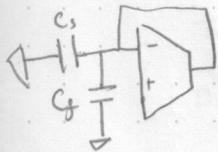d) Noise charge $V_x \rightarrow$ thermal noise integrated on C_f & C_s



$$\overline{g_x^2} = kT(C_s + C_f) \quad \text{equipartition theorem}$$

$$\overline{g_x} = k \cdot 300K \cdot 3pF = 1.24e^{-32} C^2 = \boxed{111 aC_{rms}}$$

$$e) \quad N_{A_0} = \frac{4kTR \Delta f}{G_m} \quad A_{CL}^2 \quad A_{CL} = \frac{A}{1+A\beta} \Rightarrow \frac{1}{\beta} \quad \beta = \frac{C_f}{C_s + C_f} = \frac{1}{3}$$

$$K = -\frac{C_s}{C_s + C_f}$$

$$A_{CL} = \frac{K}{\beta} = -\frac{C_f}{C_s}$$

$$N_A = \frac{4kTR \Delta f}{G_m} \cdot \left(-\frac{C_f}{C_s}\right)^2$$

$$R_0 = \frac{1}{\beta G_m} \quad \overline{i_o^2} = \alpha \cdot 4kTR G_m \Delta f$$

$$\frac{\overline{V_o^2}}{\Delta f} = \frac{4kTR}{\beta R} \cdot \left(\frac{R}{1+j\omega C_L}\right)^2$$

$$\overline{V_o^2} = \int_0^\infty \frac{4kTR}{\beta R} \left(\frac{R}{1+j\omega C_L}\right)^2 \Delta f df = \frac{4kTR}{\beta R} \cdot \int_0^\infty \frac{1}{R} \left(\frac{R}{1+j\omega C_L}\right)^2 df df$$

$$\overline{V_o^2} = \frac{4kTR}{\beta C_L}$$

$$C_{Lr} = C_L \parallel C_f = C_L + C_f = 2pF + 1pF = 3pF$$

$$\overline{V_o^2} = \frac{1 \cdot k \cdot 300K \cdot 3}{\frac{1}{3} \cdot 3pF} = 12.42 mV^2 = \boxed{111.5 \mu V_{rms}}$$

$$f) \quad \overline{V_{o1}^2} = \frac{\overline{g_x^2}}{C_f^2} = \frac{1.24e^{-32} C^2}{1pF^2} = 12.42 mV^2 = 111.5 \mu V_{rms}$$

$$\overline{V_{o_{tot}}^2} = \overline{V_{o1}^2} + \overline{V_{o2}^2} = 2\overline{V_o^2} = 24.84 \mu V^2 = \boxed{157.6 \mu V_{rms}}$$

All of the charge error in the circuit will be forced to the output by the feedback action of the amplifier, regardless of CDS action.

s) a)

1) Total noise = $1.862e^{-16}$ C_{rms}

98.5% of total noise = $1.8247e^{-16}$ C_{rms} occurs at 773 MHz

2) S/N noise = 0

Total noise = $1.813e^{-16}$ C_{rms}

Drop of 2.6 dB compared to baseline

3) to-phase = 2 S/N noise = 1 mode / V_o

Total noise 118.7 μV_{RMS}

4) Total output noise = $\sqrt{\frac{\overline{g_m^2}}{C_S^2} + \overline{V_{O_2}^2}} = \sqrt{\left(\frac{1.862e^{-16}}{1pF}\right)^2 + (118.7e^{-6V})^2}$
= 220.8 μV_{RMS}

This is 42% higher than the noise calculated in step f of problem 4

b) 1) flicker-on = 0 cds-en = 1

Total integrated noise 214.1 μV_{RMS}

2) flicker-on = 1 cds-en = 1

Total integrated noise 216.2 μV_{RMS}

No flicker noise evident in plot

3) flicker-on = 1 cds-en = 0

Total integrated noise 157.2 μV_{RMS}


Flicker noise very evident in ASD

4) flicker-on = 0 cds-on = 0

Total integrated noise 156 μV_{RMS}

Expressions

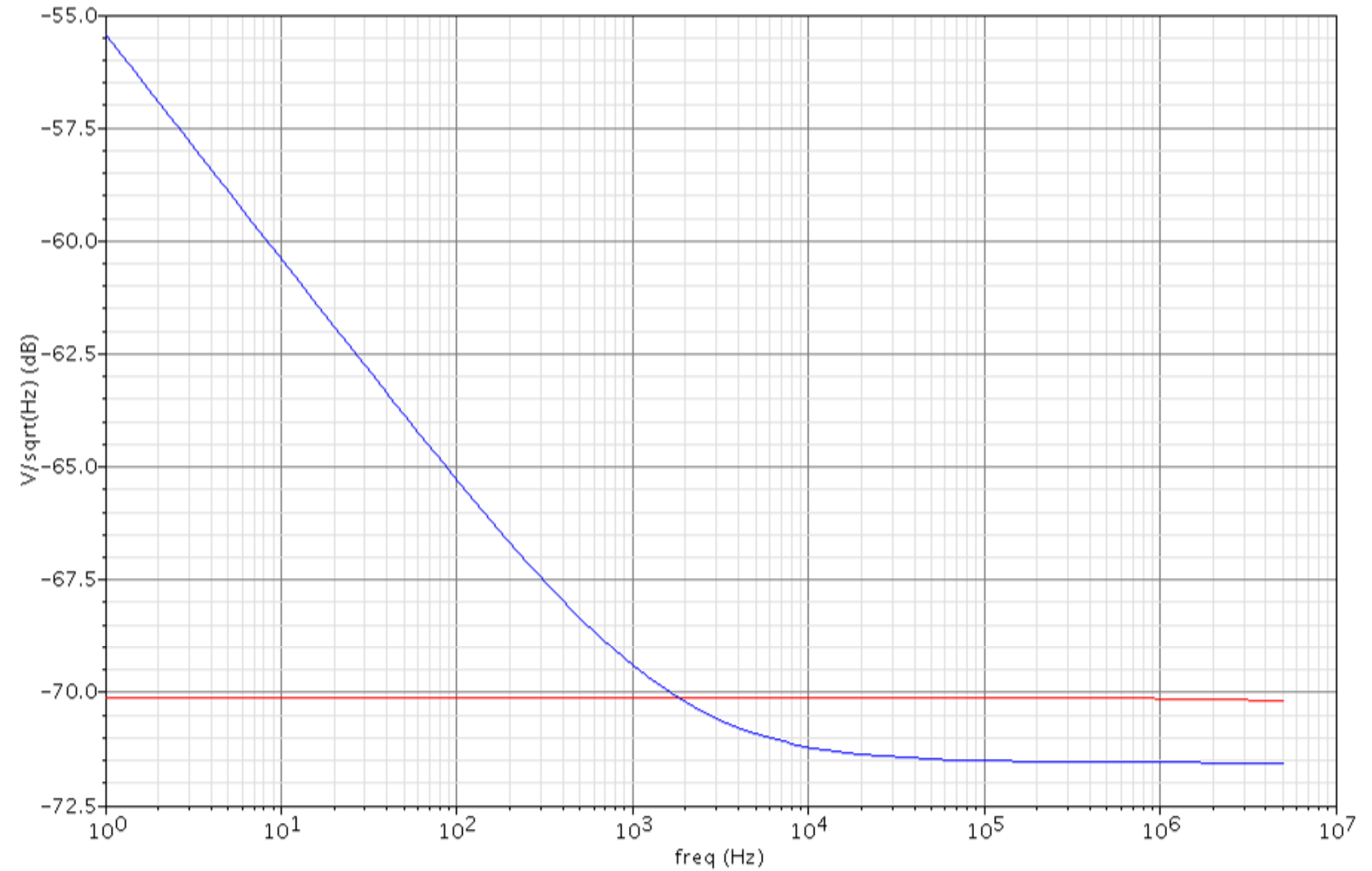— HW4 Q5 P2 Noise PSD (V/Hz) — HW4 Q5 P3 Noise PSD (V/Hz)




6) Calculate V_o at $t = t_{end}$

$A_{ol} = \infty$ switches ideal

Cases:	S_2	S_4	S_{13}	S_{14}	S_{23}	S_{12+}
0	0	0	0	0	0	0
1	0	0	1	1	0	1
2	0	0	0	0	0	0
3	1	0	0	0	1	1
4	0	0	0	0	0	0
5	0	0	1	0	1	0
6	0	0	0	0	0	0
7	0	1	0	1	0	1

Circuit 0, 2, 4, 6

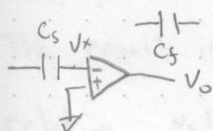

$$Q = V \cdot C$$

$$V_f = V(C_f)$$

$$V_s = V(C_s)$$

$$Q_f = V_f \cdot C_f$$

$$Q_s = V_s \cdot C_s$$

Case 1

$$V_i = 1V$$

$$V_x = 0V$$

$$V_f = 0$$

$$V_s = V_i - V_x = V_i$$

$$Q_f = 0$$

$$Q_{s1} = V_i \cdot C_s$$

Case 3


$$Q_{f1} = 0$$

$$Q_{s1} = V_i \cdot C_s$$

$$V_x \Rightarrow 0$$


$$Q_{f3} = Q_{s1} = V_i \cdot C_s$$

Circuit 3

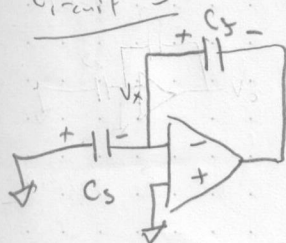

6) Cont'd

Circuit 5

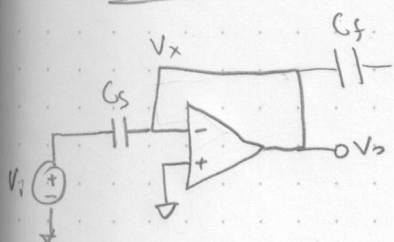


$$Q_{+3} = V_i C_s \quad Q_{S3} = 0$$

$$V_x = 0 \quad V_s = V_i - V_x = V_i$$

$$Q_{S5} = V_i C_s \quad Q_{+5} = Q_{+3} = V_i C_s$$

Circuit 7

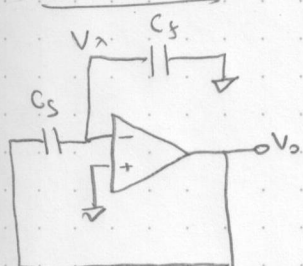

$$Q_{S5} = V_i C_s \quad Q_{S5} = V_i C_s$$

$$V_x \Rightarrow 0, \quad Q_S \rightarrow C_s$$

$$Q_S = 2 \cdot V_i C_s \quad Q = V \cdot C \Rightarrow V = \frac{Q}{C}$$

$$V_o = \frac{Q_S}{C_s} = \frac{2V_i C_s}{C_s} = 2 \cdot V_i$$

The result is interesting because first, it's not dependent on the relative values of C_s and C_s , that is, C_s and C_s don't appear in the gain equation. Second it's interesting because it's non-inverting. If the switches are good and the capacitors aren't leaky this is a neat way to get a precision gain as the component values don't matter.